

Name: Omar Ahmed Gamal
Email: omar.ahmed.ga.04@gmail.com

Project 1 (DSP48A1)

1-RTL code:

- 1) The design of the register followed by mux whose selector is a parameter:

```
reg_mux_input.v > reg_mux_input
1  module reg_mux_input(in,clk,rst,ce,out);
2  parameter SELECTOR=1;
3  parameter INPUT_WIDTH=18;
4  parameter RSTTYPE="SYNC";
5      input  clk, rst, ce;
6      input  [INPUT_WIDTH-1:0] in;
7      output [INPUT_WIDTH-1:0] out;
8
9      reg [INPUT_WIDTH-1:0] q;
10 generate
11     if(RSTTYPE == "SYNC") begin
12         always @(posedge clk) begin
13             if (rst) begin
14                 q <= 0;
15             end else if (ce) begin
16                 q <= in;
17             end
18         end
19     end else if (RSTTYPE == "ASYNC") begin
20         always @(posedge clk or posedge rst) begin
21             if (rst) begin
22                 q <= 0;
23             end else if (ce) begin
24                 q <= in;
25             end
26         end
27     end else begin
28         always @(posedge clk) begin
29             if (rst) begin
30                 q <= 0;
31             end else if (ce) begin
32                 q <= in;
33             end
34         end
35     end
36 endgenerate
37 assign out = (SELECTOR == 1) ? q : in;
38
```

- 2) The DSP48A1 top module (which is the main design):

```

DSP48A1_TOP.V > DSP48A1
module DSP48A1(A,B,C,D,CLK,CARRYIN,OPMODE,BCIN,RSTA,RSTB,RSTM,RSTP,RSTC,RSTD,RSTCARRYIN,RSTOPMODE,CEA,CEB,CEM,CEP,CEC,CED,CECARRYIN,CEOPMODE,
PCIN,BCOUT,PCOUT,P,M,CARRYOUT,CARRYOUTF);
parameter A0REG=0;
parameter A1REG=1;
parameter B0REG=0;
parameter B1REG=1;
parameter CREG=1;
parameter DREG=1;
parameter PREG=1;
parameter MREG=1;
parameter CARRYINREG=1;
parameter OPMODEREG=1;
parameter CARRYOUTREG=1;
parameter CARRYINSEL="OPMODE5";
parameter B_INPUT="DIRECT";
parameter RSTTYPE="SYNC";
input [17:0] A, B, D;
input [47:0] C;
input CLK, CARRYIN, RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE, CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
input [7:0] OPMODE;
input [17:0] BCIN;
input [47:0] PCIN;
output [47:0] PCOUT;
output [17:0] BCOUT;
output [47:0] P;
output [35:0] M;
output CARRYOUT, CARRYOUTF;
wire [17:0] a0reg_out, a1reg_out;
wire [17:0] b0reg_out, b1reg_out, mux_bcascade_out;
wire [47:0] creg_out;
wire [17:0] dreg_out;
wire [7:0] opmodereg_out;
wire [35:0] mreg_out;
wire [47:0] DAB_concatenated;
wire carrycascade_out;
wire carryinreg_out;
wire carryoutreg_out;
wire [47:0] preg_out;
wire [47:0] mreg_extended_out;
reg [17:0] preaddsub_out;
reg [17:0] mux_preadsub_out;
reg [35:0] mul_out;
reg [47:0] mux_x_out;
reg [47:0] mux_z_out;
reg [47:0] postaddsub_out;
reg carryout postaddsub;
assign mux_bcascade_out = (B_INPUT == "DIRECT") ? B : (B_INPUT == "CASCADE") ? BCIN : 18'b0; // MUX THAT INDICATES THE INPUT FOR B0REG
assign carrycascade_out = (CARRYINSEL == "OPMODE5") ? opmodereg_out[5] : (CARRYINSEL == "CARRYIN") ? CARRYIN : 1'b0; // MUX THAT INDICATES THE INPUT FOR CARRYINREG
assign M=mreg_out;
assign P=preg_out;
assign PCOUT = preg_out;
assign mreg_extended_out = {12'b0,mreg_out}; // Extend MREG to 48 bits to enter the x mux with 48bit output
assign BCOUT = b1reg_out;
assign CARRYOUT = carryoutreg_out;
assign CARRYOUTF = CARRYOUT; // CARRYOUTF is the same as CARRYOUT in DSP48A1
assign DAB_concatenated={dreg_out[11:0],a1reg_out[17:0],b1reg_out[17:0]}; // Concatenate 48 bits

```

```

// Instantiate the input registers based on the parameters
//A0REG
reg_mux_input #(.SELECTOR(A0REG), .INPUT_WIDTH(18), .RSTTYPE(RSTTYPE)) a0reg (
    .in(A),
    .clk(CLK),
    .rst(RSTA),
    .ce(CEA),
    .out(a0reg_out)
);
//A1REG
reg_mux_input #(.SELECTOR(A1REG), .INPUT_WIDTH(18), .RSTTYPE(RSTTYPE)) a1reg (
    .in(a0reg_out),
    .clk(CLK),
    .rst(RSTA),
    .ce(CEA),
    .out(a1reg_out)
);
//B0REG
reg_mux_input #(.SELECTOR(B0REG), .INPUT_WIDTH(18), .RSTTYPE(RSTTYPE)) b0reg (
    .in(mux_bascade_out),
    .clk(CLK),
    .rst(RSTB),
    .ce(CEB),
    .out(b0reg_out)
);
//B1REG
reg_mux_input #(.SELECTOR(B1REG), .INPUT_WIDTH(18), .RSTTYPE(RSTTYPE)) b1reg (
    .in(mux_preaddsub_out),
    .clk(CLK),
    .rst(RSTB),
    .ce(CEB),
    .out(b1reg_out)
);
//CREG
reg_mux_input #(.SELECTOR(CREG), .INPUT_WIDTH(48), .RSTTYPE(RSTTYPE)) creg (
    .in(C),
    .clk(CLK),
    .rst(RSTC),
    .ce(CEC),
    .out(creg_out)
);
//DREG
reg_mux_input #(.SELECTOR(DREG), .INPUT_WIDTH(18), .RSTTYPE(RSTTYPE)) dreg (
    .in(D),
    .clk(CLK),
    .rst(RSTD),
    .ce(CED),
    .out(dreg_out)
);
//OPMODEREG
reg_mux_input #(.SELECTOR(OPMODEREG), .INPUT_WIDTH(8), .RSTTYPE(RSTTYPE)) opmodereg (
    .in(OPMODE),
    .clk(CLK),
    .rst(RSTOPMODE),
    .ce(CEOPMODE),
    .out(opmodereg_out)
);
//MREG
reg_mux_input #(.SELECTOR(MREG), .INPUT_WIDTH(36), .RSTTYPE(RSTTYPE)) mreg (
    .in(mul_out),
    .clk(CLK),
    .rst(RSTM),
    .ce(CEM),
    .out(mreg_out)
);
//CARRYINREG
reg_mux_input #(.SELECTOR(CARRYINREG), .INPUT_WIDTH(1), .RSTTYPE(RSTTYPE)) carryinreg (
    .in(carrycascade_out),
    .clk(CLK),
    .rst(RSTCARRYIN),
    .ce(CECARRYIN),
    .out(carryinreg_out)
);
//CARRYOUTREG
reg_mux_input #(.SELECTOR(CARRYOUTREG), .INPUT_WIDTH(1), .RSTTYPE(RSTTYPE)) carryoutreg (
    .in(carryout_postaddsub),
    .clk(CLK),
    .rst(RSTCARRYIN),
    .ce(CECARRYIN),
    .out(carryoutreg_out)
);
//PREG
reg_mux_input #(.SELECTOR(PREG), .INPUT_WIDTH(48), .RSTTYPE(RSTTYPE)) preg (
    .in(postaddsub_out),
    .clk(CLK),
    .rst(RSTP),
    .ce(CEP),
    .out(preg_out)
);

```

```

always @(dreg_out or b0reg_out or opmodereg_out[6] or opmodereg_out[4] or b1reg_out or a1reg_out) begin
    case (opmodereg_out[6])
        1'b0: preaddsub_out = dreg_out + b0reg_out; // ADD
        1'b1: preaddsub_out = dreg_out - b0reg_out; // SUB
    endcase
    if (opmodereg_out[4]) begin
        mux_preadsub_out = preaddsub_out; // If OPMODE[4]=1, use the preaddsub_out
    end else begin
        mux_preadsub_out = b0reg_out; // Otherwise, use b0reg_out
    end
    mul_out = a1reg_out * b1reg_out; // Perform multiplication
end

always @(preg_out or DAB_concatenated or mreg_extended_out or creg_out or PCIN or opmodereg_out [3:0] or carryinreg_out) begin
    //multiplexior X
    case (opmodereg_out[1:0])
        2'b00: mux_x_out = 48'h0; // 0
        2'b01: mux_x_out = mreg_extended_out; // multiplier output
        2'b10: mux_x_out = preg_out; // PREG output
        2'b11: mux_x_out = DAB_concatenated; // Concatenated DAB
    endcase
    //multiplexior Z
    case (opmodereg_out[3:2])
        2'b00: mux_z_out = 48'h0; // 0
        2'b01: mux_z_out = PCIN; // PCIN input
        2'b10: mux_z_out = preg_out; // PREG output
        2'b11: mux_z_out = creg_out; // CREG output
    endcase
    //postaddsub_out
    if (!opmodereg_out[7]) begin
        {carryout_postaddsub, postaddsub_out} = mux_x_out + mux_z_out + carryinreg_out; // If OPMODE[7]=0, perform addition
    end else begin
        {carryout_postaddsub, postaddsub_out} = mux_z_out - (mux_x_out + carryinreg_out); // Otherwise, perform subtraction
    end
end

endmodule

```

2-Testbench code:

```
DSP48A1_tb.v > DSP48A1.tb
module DSP48A1_tb ();
// parameters added if needed to change them
parameter A0REG=0;parameter A1REG=1;parameter B0REG=0;parameter B1REG=1;
parameter CREG=1;parameter DREG=1;parameter PREG=1;parameter MREG=1;
parameter CARRYINREG=1;parameter OPMODEREG=1;parameter CARRYOUTREG=1;
parameter CARRYINSEL="OPMODES";parameter B_INPUT="DIRECT";parameter RSTTYPE="SYNC";
//input signals
reg [17:0] A, B, D;
reg [47:0] C;
reg CLK, CARRYIN, RSTA, RSTB, RSTM, RSTP, RSTC, RSTD, RSTCARRYIN, RSTOPMODE;
reg CEA, CEB, CEM, CEP, CEC, CED, CECARRYIN, CEOPMODE;
reg [7:0] OPMODE;
reg [17:0] BCIN;
reg [47:0] PCIN;
//output signals
wire [17:0] BCOUT;
wire [47:0] PCOUT;
wire [47:0] P;
wire [35:0] M;
wire CARRYOUT, CARRYOUTF;

reg [47:0] past_p_out;
reg past_carryout_out;
// Instantiate the DSP48A1_TOP module
DSP48A1 #(
    .A0REG(A0REG), .A1REG(A1REG), .B0REG(B0REG), .B1REG(B1REG),
    .CREG(CREG), .DREG(DREG), .PREG(PREG), .MREG(MREG),
    .CARRYINREG(CARRYINREG), .OPMODEREG(OPMODEREG), .CARRYOUTREG(CARRYOUTREG),
    .CARRYINSEL(CARRYINSEL), .B_INPUT(B_INPUT), .RSTTYPE(RSTTYPE)
) DUT (
    .A(A), .B(B), .C(C), .D(D),
    .CLK(CLK), .CARRYIN(CARRYIN),
    .OPMODE(OPMODE), .BCIN(BCIN),
    .RSTA(RSTA), .RSTB(RSTB), .RSTM(RSTM),
    .RSTP(RSTP), .RSTC(RSTC), .RSTD(RSTD),
    .RSTCARRYIN(RSTCARRYIN), .RSTOPMODE(RSTOPMODE),
    .CEA(CEA), .CEB(CEB), .CEM(CEM),
    .CEP(CEP), .CEC(CEC), .CED(CED),
    .CECARRYIN(CECARRYIN), .CEOPMODE(CEOPMODE),
    .PCIN(PCIN),
    .BCOUT(BCOUT),
    .PCOUT(PCOUT),
    .P(P),
    .M(M),
    .CARRYOUT(CARRYOUT),
    .CARRYOUTF(CARRYOUTF)
);
// clock generation
initial begin
    CLK = 0;
    forever #1 CLK = ~CLK;
end
```

Verify Reset Operation:

```
//test module
initial begin
    //test 1: Verify Reset Operation
    RSTA = 1; RSTB = 1; RSTM = 1; RSTP = 1; RSTC = 1; RSTD = 1; RSTCARRYIN = 1; RSTOPMODE = 1; // Assert all resets by setting them 1
    A=$random; B=$random; C=$random; D=$random; OPMODE=$random; BCIN=$random; PCIN=$random; CARRYIN=$random;
    CEA=$random; CEB=$random; CEM=$random; CEP=$random; CEC=$random; CED=$random; CECARRYIN=$random; CEOPMODE=$random; //Drive remaining inputs with (random) values.
    @(negedge CLK);
    if (BCOUT!=0||PCOUT!=0||P!=0||M!=0||CARRYOUT!=0||CARRYOUTF!=0) begin
        $display("ERROR - (Verify Reset Operation test) Failed - Outputs not zero after reset");
        $stop;
    end else begin
        $display("Correct outputs - (Verify Reset Operation test) Passed - Outputs are zero after reset");
    end
    RSTA = 0; RSTB = 0; RSTM = 0; RSTP = 0; RSTC = 0; RSTD = 0; RSTCARRYIN = 0; RSTOPMODE = 0; // Deassert resets
    CEA=1; CEB=1; CEM=1; CEP=1; CEC=1; CED=1; CECARRYIN=1; CEOPMODE=1; //assert all clock enable signals
```

Verify DSP Path 1:

```
//test 2: Verify DSP Path 1
OPMODE = 8'b11011101;
A=18'd20; B=18'd10; C=48'd350; D=18'd25;
BCIN=$random; PCIN=$random; CARRYIN=$random;
repeat(4) @(negedge CLK); // Wait for 4 clock cycles
if (BCOUT!=18'hf) begin
    $display("ERROR - (verify DSP path 1 test) Failed - BCOUT output is wrong value BCOUT=%h expected= 18'hf", BCOUT);
    $stop;
end else begin
    $display("Correct BCOUT output BCOUT=%h expected= 18'hf", BCOUT);
end
if (M!=36'h12c) begin
    $display("ERROR - (verify DSP path 1 test) Failed - M output is wrong value M=%h expected= 36'h12c", M);
    $stop;
end else begin
    $display("Correct M output M=%h expected= 36'h12c", M);
end
if (P!=48'h32) begin
    $display("ERROR - (verify DSP path 1 test) Failed - P output is wrong value P=%h expected= 48'h32", P);
    $stop;
end else if (PCOUT!=P) begin
    $display("ERROR - (verify DSP path 1 test) Failed - PCOUT output is NOT equal P output value PCOUT=%h expected=%h", PCOUT, P);
    $stop;
end else begin
    $display("Correct P and PCOUT output values P=%h PCOUT=%h expected= 48'h32", P, PCOUT);
end
if (CARRYOUT!=1'b0) begin
    $display("ERROR - (verify DSP path 1 test) Failed - CARRYOUT output is wrong value CARRYOUT=%b expected= 1'b0", CARRYOUT);
    $stop;
end else if (CARRYOUTF!=CARRYOUT) begin
    $display("ERROR - (verify DSP path 1 test) Failed - CARRYOUTF output is NOT equal CARRYOUT output value CARRYOUTF=%b expected= %b", CARRYOUTF, CARRYOUT);
end else begin
    $display("Correct CARRYOUT and CARRYOUTF output values CARRYOUT=%b CARRYOUTF=%b expected= 1'b0", CARRYOUT, CARRYOUTF);
end
$display("Correct outputs - (Verify DSP Path 1 test) Passed - Outputs are correct after DSP path 1 operation");
```

Verify DSP Path 2:

```
//test 2: Verify DSP Path 2
OPMODE=8'b00010000;
A=18'd20; B=18'd10; C=48'd350; D=18'd25;
BCIN=$random; PCIN=$random; CARRYIN=$random;
repeat(3) @(negedge CLK); // Wait for 3 clock cycles
if (BCOUT!=18'h23) begin
    $display("ERROR - (verify DSP path 2 test) Failed - BCOUT output is wrong value BCOUT=%h expected= 18'h23", BCOUT);
    $stop;
end else begin
    $display("Correct BCOUT output BCOUT=%h expected= 18'h23", BCOUT);
end
if (M!=36'h2bc) begin
    $display("ERROR - (verify DSP path 2 test) Failed - M output is wrong value M=%h expected= 36'h2bc", M);
    $stop;
end else begin
    $display("Correct M output M=%h expected= 36'h2bc", M);
end
if (P!=48'h0) begin
    $display("ERROR - (verify DSP path 2 test) Failed - P output is wrong value P=%h expected= 48'h0", P);
    $stop;
end else if (PCOUT!=P) begin
    $display("ERROR - (verify DSP path 2 test) Failed - PCOUT output is NOT equal P output value PCOUT=%h expected=%h", PCOUT, P);
    $stop;
end else begin
    $display("Correct P and PCOUT output values P=%h PCOUT=%h expected= 48'h0", P, PCOUT);
end
if (CARRYOUT!=1'b0) begin
    $display("ERROR - (verify DSP path 2 test) Failed - CARRYOUT output is wrong value CARRYOUT=%b expected= 1'b0", CARRYOUT);
    $stop;
end else if (CARRYOUTF!=CARRYOUT) begin
    $display("ERROR - (verify DSP path 2 test) Failed - CARRYOUTF output is NOT equal CARRYOUT output value CARRYOUTF=%b expected= %b", CARRYOUTF, CARRYOUT);
end else begin
    $display("Correct CARRYOUT and CARRYOUTF output values CARRYOUT=%b CARRYOUTF=%b expected= 1'b0", CARRYOUT, CARRYOUTF);
end
$display("Correct outputs - (Verify DSP Path 2 test) Passed - Outputs are correct after DSP path 2 operation");
```

Verify DSP Path 3:

```
//test 4: Verify DSP Path 3
OPMODE=8'b00001010;
A=18'd20; B=18'd10; C=48'd350; D=18'd25;
BCIN=$random; PCIN=$random; CARRYIN=$random;
past_p_out = P; // Store the previous P output value
past_carryout_out = CARRYOUT; // Store the previous CARRYOUT output value
repeat(3) @(negedge CLK); // Wait for 3 clock cycles
if (BCOUT!=18'ha) begin
    $display("ERROR - (verify DSP path 3 test) Failed - BCOUT output is wrong value BCOUT=%h expected= 18'ha", BCOUT);
    $stop;
end else begin
    $display("Correct BCOUT output BCOUT=%h expected= 18'ha", BCOUT);
end
if (M!=36'hc8) begin
    $display("ERROR - (verify DSP path 3 test) Failed - M output is wrong value M=%h expected= 36'hc8", M);
    $stop;
end else begin
    $display("Correct M output M=%h expected= 36'hc8", M);
end
if (P!=past_p_out) begin
    $display("ERROR - (verify DSP path 3 test) Failed - P output is wrong value P=%h expected= %h", P, past_p_out);
    $stop;
end else if (PCOUT!=P) begin
    $display("ERROR - (verify DSP path 3 test) Failed - PCOUT output is NOT equal P output value PCOUT=%h expected=%h", PCOUT, P);
    $stop;
end else begin
    $display("Correct P and PCOUT output values P=%h PCOUT=%h expected=%h", P, PCOUT, past_p_out);
end
if (CARRYOUT!=past_carryout_out) begin
    $display("ERROR - (verify DSP path 3 test) Failed - CARRYOUT output is wrong value CARRYOUT=%b expected= %b", CARRYOUT, past_carryout_out);
    $stop;
end else if (CARRYOUTF!=CARRYOUT) begin
    $display("ERROR - (verify DSP path 3 test) Failed - CARRYOUTF output is NOT equal CARRYOUT output value CARRYOUTF=%b expected= %b", CARRYOUTF, CARRYOUT);
end else begin
    $display("Correct CARRYOUT and CARRYOUTF output values CARRYOUT=%b CARRYOUTF=%b expected= %b", CARRYOUT, CARRYOUTF, past_carryout_out);
end
$display("Correct outputs - (Verify DSP Path 3 test) Passed - Outputs are correct after DSP path 3 operation");
```

Verify DSP Path 4:

```
//test 5: Verify DSP Path 4
OPMODE=8'b10100111;
A=18'd5; B=18'd6; C=48'd350; D=18'd25;
BCIN=$random; PCIN=48'd3000; CARRYIN=$random;
repeat(3) @(negedge CLK); // Wait for 3 clock cycles
if (BCOUT!=18'h6) begin
    $display("ERROR - (verify DSP path 4 test) Failed - BCOUT output is wrong value BCOUT=%h expected= 18'h6", BCOUT);
    $stop;
end else begin
    $display("Correct BCOUT output BCOUT=%h expected= 18'h6", BCOUT);
end
if (M!=36'h1e) begin
    $display("ERROR - (verify DSP path 4 test) Failed - M output is wrong value M=%h expected= 36'h1e", M);
    $stop;
end else begin
    $display("Correct M output M=%h expected= 36'h1e", M);
end
if (P!=48'hfe6ffec0bb1) begin
    $display("ERROR - (verify DSP path 4 test) Failed - P output is wrong value P=%h expected= %h", P, 48'hfe6ffec0bb1);
    $stop;
end else if (PCOUT!=P) begin
    $display("ERROR - (verify DSP path 4 test) Failed - PCOUT output is NOT equal P output value PCOUT=%h expected=%h", PCOUT, P);
    $stop;
end else begin
    $display("Correct P and PCOUT output values P=%h PCOUT=%h expected=%h", P, PCOUT, 48'hfe6ffec0bb1);
end
if (CARRYOUT!=1'b1) begin
    $display("ERROR - (verify DSP path 4 test) Failed - CARRYOUT output is wrong value CARRYOUT=%b expected= %b", CARRYOUT, 1'b1);
    $stop;
end else if (CARRYOUTF!=CARRYOUT) begin
    $display("ERROR - (verify DSP path 4 test) Failed - CARRYOUTF output is NOT equal CARRYOUT output value CARRYOUTF=%b expected= %b", CARRYOUTF, CARRYOUT);
end else begin
    $display("Correct CARRYOUT and CARRYOUTF output values CARRYOUT=%b CARRYOUTF=%b expected= %b", CARRYOUT, CARRYOUTF, 1'b1);
end
$display("Correct outputs - (Verify DSP Path 4 test) Passed - Outputs are correct after DSP path 4 operation");
$display("ALL tests are passed");
$stop;
end
endmodule
```



3-DO file:



```
run.do
1 vlib work
2 vlog reg_mux_input.v DSP48A1_TOP.V DSP48A1_tb.v
3 vsim -voptargs=+acc work.DSP48A1_tb
4 add wave *
5 run -all
```


do run.do

VISIM 8> do run.do

4- QuestaSim Snippets:

 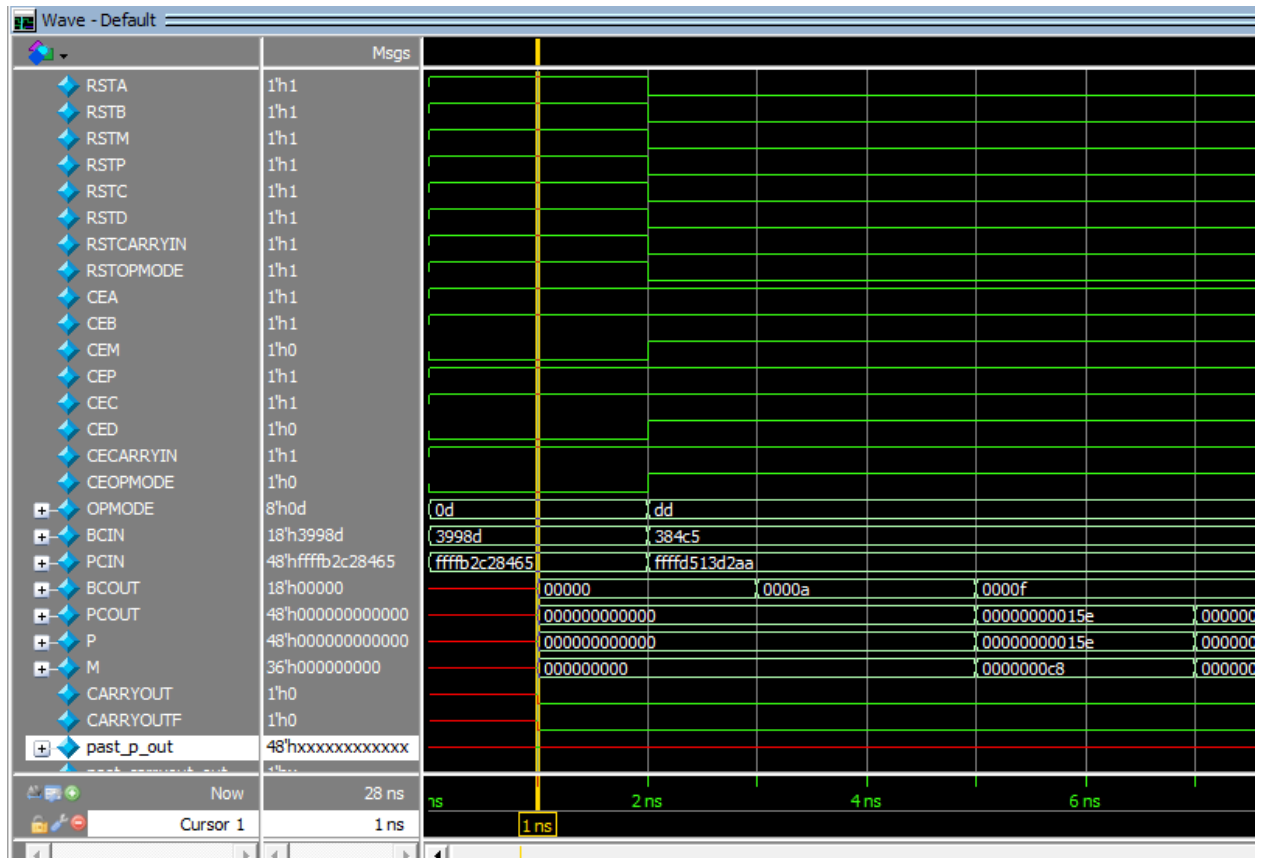

 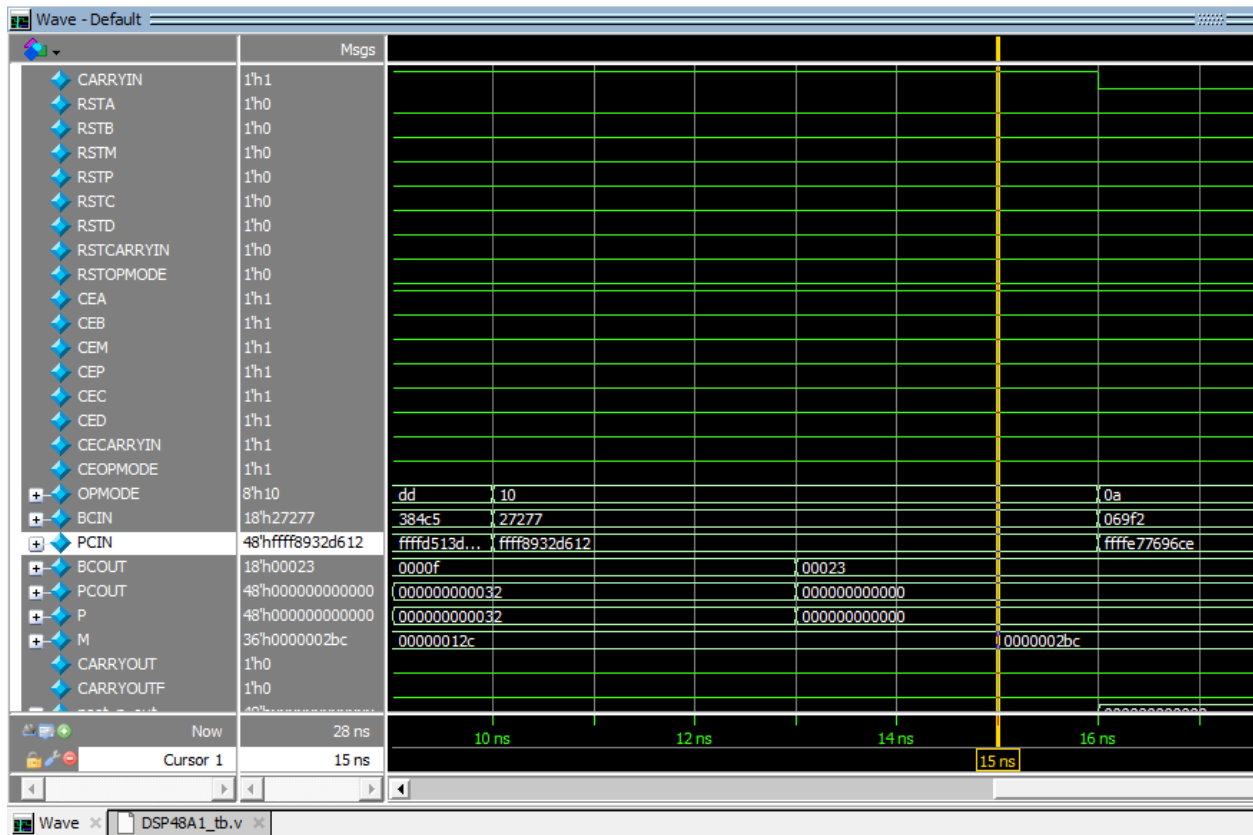

 

```

QuestaSim> do run.do
# ** Warning: (vlib-34) Library already exists at "work".
# Errors: 0, Warnings: 1
# QuestaSim-64 vlog 2021.1 Compiler 2021.01 Jan 19 2021
# Start time: 22:31:33 on Aug 03,2025
# vlog -reportprogress 300 reg_mux_input.v DSP48A1_TOP.V DSP48A1_tb.v
# -- Compiling module reg_mux_input
# -- Compiling module DSP48A1
# -- Compiling module DSP48A1_tb
#
# Top level modules:
#   DSP48A1_tb
# End time: 22:31:33 on Aug 03,2025, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
# vsim -voptargs="+acc" work.DSP48A1_tb
# Start time: 22:31:33 on Aug 03,2025
# ** Note: (vsim-3813) Design is being optimized due to module recompilation...
# Loading work.DSP48A1_tb(fast)
# Loading work.DSP48A1(fast)
# Loading work.reg_mux_input(fast)
# Loading work.reg_mux_input(fast_1)
# Loading work.reg_mux_input(fast_2)
# Loading work.reg_mux_input(fast_3)
# Loading work.reg_mux_input(fast_4)
# Loading work.reg_mux_input(fast_5)
# Correct outputs - (Verify Reset Operation test) Passed - Outputs are zero after reset
# Correct BCOUT output BCOUT=0000f expected= 18'hf
# Correct M output M=00000012c expected= 36'h12c
# Correct P and PCOUT output values P=0000000000032 PCOUT=0000000000032 expected= 48'h32
# Correct CARRYOUT and CARRYOUTF output values CARRYOUT=0 CARRYOUTF=0 expected= 1'b0
# Correct outputs - (Verify DSP Path 1 test) Passed - Outputs are correct after DSP path 1 operation
# Correct BCOUT output BCOUT=00023 expected= 18'h23
# Correct M output M=0000002bc expected= 36'h2bc
# Correct P and PCOUT output values P=0000000000000 PCOUT=0000000000000 expected= 48'h0
# Correct CARRYOUT and CARRYOUTF output values CARRYOUT=0 CARRYOUTF=0 expected= 1'b0
# Correct outputs - (Verify DSP Path 2 test) Passed - Outputs are correct after DSP path 2 operation
# Correct BCOUT output BCOUT=0000a expected= 18'ha
# Correct M output M=0000000c8 expected= 36'hc8
# Correct P and PCOUT output values P=0000000000000 PCOUT=0000000000000 expected= 0000000000000
# Correct CARRYOUT and CARRYOUTF output values CARRYOUT=0 CARRYOUTF=0 expected= 0
# Correct outputs - (Verify DSP Path 3 test) Passed - Outputs are correct after DSP path 3 operation
# Correct BCOUT output BCOUT=00006 expected= 18'h6
# Correct M output M=00000001e expected= 36'h1e
# Correct P and PCOUT output values P=fe6fffec0bb1 PCOUT=fe6fffec0bb1 expected=fe6fffec0bb1
# Correct CARRYOUT and CARRYOUTF output values CARRYOUT=1 CARRYOUTF=1 expected= 1
# Correct outputs - (Verify DSP Path 4 test) Passed - Outputs are correct after DSP path 4 operation
# ALL tests are passed
# ** Note: $stop : DSP48A1_tb.v(220)
# Time: 28 ns Iteration: 1 Instance: /DSP48A1_tb
# Break in Module DSP48A1_tb at DSP48A1_tb.v line 220

```

5-Constraint File :


```
## This file is a general .xdc for the Basys3 rev B board
## To use it in a project:
## - uncomment the lines corresponding to used pins
## - rename the used ports (in each line, after get_ports) according to the top level signal names in the project

## Clock signal
set_property -dict { PACKAGE_PIN W5    IOSTANDARD LVCMOS33 } [get_ports CLK]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports CLK]

## Switches
#set_property -dict { PACKAGE_PIN V17    IOSTANDARD LVCMOS33 } [get_ports {sw[0]}]
#set_property -dict { PACKAGE_PIN V16    IOSTANDARD LVCMOS33 } [get_ports {sw[1]}]
#set_property -dict { PACKAGE_PIN W16    IOSTANDARD LVCMOS33 } [get_ports {sw[2]}]
#set_property -dict { PACKAGE_PIN W17    IOSTANDARD LVCMOS33 } [get_ports {sw[3]}]
#set_property -dict { PACKAGE_PIN W15    IOSTANDARD LVCMOS33 } [get_ports {sw[4]}]
#set_property -dict { PACKAGE_PIN V15    IOSTANDARD LVCMOS33 } [get_ports {sw[5]}]
#set_property -dict { PACKAGE_PIN W14    IOSTANDARD LVCMOS33 } [get_ports {sw[6]}]
#set_property -dict { PACKAGE_PIN W13    IOSTANDARD LVCMOS33 } [get_ports {sw[7]}]
#set_property -dict { PACKAGE_PIN V2     IOSTANDARD LVCMOS33 } [get_ports {sw[8]}]
#set_property -dict { PACKAGE_PIN T3     IOSTANDARD LVCMOS33 } [get_ports {sw[9]}]
#set_property -dict { PACKAGE_PIN T2     IOSTANDARD LVCMOS33 } [get_ports {sw[10]}]
#set_property -dict { PACKAGE_PIN R3     IOSTANDARD LVCMOS33 } [get_ports {sw[11]}]
#set_property -dict { PACKAGE_PIN W2     IOSTANDARD LVCMOS33 } [get_ports {sw[12]}]
#set_property -dict { PACKAGE_PIN U1     IOSTANDARD LVCMOS33 } [get_ports {sw[13]}]
#set_property -dict { PACKAGE_PIN T1     IOSTANDARD LVCMOS33 } [get_ports {sw[14]}]
#set_property -dict { PACKAGE_PIN R2     IOSTANDARD LVCMOS33 } [get_ports {sw[15]}]
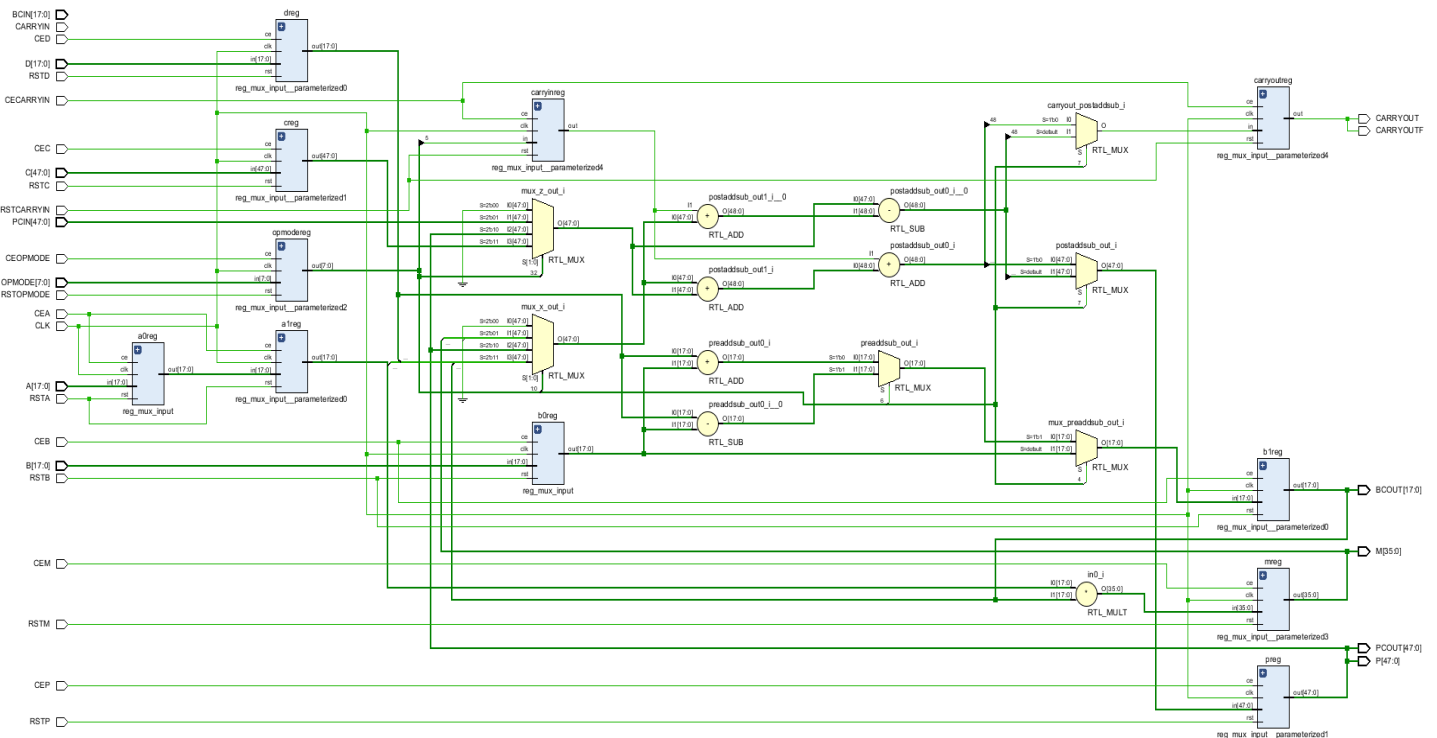
## LEDs
#set_property -dict { PACKAGE_PIN U16    IOSTANDARD LVCMOS33 } [get_ports {led[0]}]
```

6-Elaboration (“Messages” tab & Schematic snippets) :



Tcl ConsoleMessages x LogReportsDesign RunsTiming

Warning (24)

Info (118)

Status (242)

Show All

Vivado Commands (3 infos)

General Messages (3 infos)

[IP_Flow 19-234] Refreshing IP repositories

[IP_Flow 19-1704] No user IP repositories specified

[IP_Flow 19-2313] Loaded Vivado IP repository 'C:/xilinx/Vivado/2018.2/data/ip'

Elaborated Design (23 warnings, 17 infos)

General Messages (23 warnings, 17 infos)

[Synth 8-2490] overwriting previous definition of module DSP48A1 [DSP48A1_TOP.V:1]

[Synth 8-6157] synthesizing module 'DSP48A1' [DSP48A1_TOP.V:1] (6 more like this)

Tcl ConsoleMessagesLogReportsDesign RunsTiming x

Design Timing Summary

General Information

Timer Settings

Design Timing Summary

Clock Summary (1)

Check Timing (326)

Intra-Clock Paths

Inter-Clock Paths

Other Path Groups

User Ignored Paths

Unconstrained Paths

| Setup | Hold | Pulse Width |
|--------------------------------------|----------------------------------|---|
| Worst Negative Slack (WNS): 5.219 ns | Worst Hold Slack (WHS): 0.182 ns | Worst Pulse Width Slack (WPWS): 4.500 ns |
| Total Negative Slack (TNS): 0.000 ns | Total Hold Slack (THS): 0.000 ns | Total Pulse Width Negative Slack (TPWS): 0.000 ns |
| Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 |
| Total Number of Endpoints: 87 | Total Number of Endpoints: 87 | Total Number of Endpoints: 162 |

All user specified timing constraints are met.

Tcl ConsoleMessagesLogReportsDesign RunsUtilization x Timing

Hierarchy

Hierarchy

Summary

Slice Logic

Slice LUTs (<1%)

LUT as Logic (<1%)

Slice Registers (<1%)

Register as Flip Flop (<1%)

Memory

DSP

DSPs (<1%)

DSP48E1 only

IO and GT Specific

Bonded IOB (65%)

IOB Master Pads

Clocking

BUFGCTRL (3%)

Specific Feature

Primitives

Black Boxes

Instantiated Netlists

| Name | Slice LUTs (134600) | Slice Registers (269200) | DSP s (740) | Bonded IOB (500) | BUFGCTRL (32) |
|---------------------------|------------------------|-----------------------------|-----------------------|---------------------|------------------|
| DSP48A1 | 289 | 160 | 1 | 327 | 1 |
| a1reg (reg_mux_input_... | 0 | 18 | 0 | 0 | 0 |
| b1reg (reg_mux_input_... | 0 | 18 | 0 | 0 | 0 |
| carryinreg (reg_mux_in... | 1 | 1 | 0 | 0 | 0 |
| carryoutreg (reg_mux_i... | 0 | 1 | 0 | 0 | 0 |
| creg (reg_mux_input_... | 0 | 48 | 0 | 0 | 0 |
| dreg (reg_mux_input_... | 0 | 18 | 0 | 0 | 0 |
| mreg (reg_mux_input_... | 0 | 0 | 1 | 0 | 0 |
| opmodereg (reg_mux_... | 287 | 8 | 0 | 0 | 0 |
| preg (reg_mux_input_... | 0 | 48 | 0 | 0 | 0 |

utilization_1

[illegible]

Tcl Console Messages x Log Reports Design Runs Power DRC Methodology Timing ? _ □ □

Warning (68) Info (242) Status (472) Show All

Vivado Commands (3 infos)

- General Messages (3 infos)
 - [IP_Flow 19-234] Refreshing IP repositories
 - [IP_Flow 19-1704] No user IP repositories specified
 - [IP_Flow 19-2313] Loaded Vivado IP repository 'C:/Xilinx/Vivado/2018.2/data/ip/
- Elaborated Design (23 warnings, 17 infos)
 - General Messages (23 warnings, 17 infos)
 - [Synth 8-2490] overwriting previous definition of module DSP48A1 [DSP48A1_TOP.V:1]
 - [Synth 8-6157] synthesizing module 'DSP48A1' [DSP48A1_TOP.V:1] (6 more like this)

Tcl Console Messages Log Reports Design Runs Power DRC Methodology Timing x ? _ □ □

Design Timing Summary

General Information
Timer Settings
Design Timing Summary
Clock Summary (1)
Check Timing (326)
Intra-Clock Paths
Inter-Clock Paths
Other Path Groups
User Ignored Paths
Unconstrained Paths

| Setup | Hold | Pulse Width |
|--------------------------------------|----------------------------------|---|
| Worst Negative Slack (WNS): 3.530 ns | Worst Hold Slack (WHS): 0.261 ns | Worst Pulse Width Slack (WPWS): 4.500 ns |
| Total Negative Slack (TNS): 0.000 ns | Total Hold Slack (THS): 0.000 ns | Total Pulse Width Negative Slack (TPWS): 0.000 ns |
| Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 | Number of Failing Endpoints: 0 |
| Total Number of Endpoints: 106 | Total Number of Endpoints: 106 | Total Number of Endpoints: 181 |

All user specified timing constraints are met.

Tcl Console Messages Log Reports Design Runs Power DRC Methodology Timing Utilization x ? _ □ □

Hierarchy

Hierarchy Summary

Slice Logic

- Slice LUTs (<1%)
 - LUT as Logic (<1%)
- Slice Registers (<1%)
 - Register as Flip Flop (<1%)
- Slice Logic Distribution
 - Slice (1%)
 - SLICEM
 - SLICEL
 - LUT Flip Flop Pairs (<1%)
 - LUT-FF pairs with one unused LUT
 - fully used LUT-FF pairs
 - LUT-FF pairs with one unused Flip Flop
 - LUT as Logic (<1%)
 - using O5 and O6
 - using O6 output only
- Memory

| Name | Slice LUTs (133800) | Slice Registers (267600) | Slice (33450) | LUT as Logic (133800) | LUT Flip Flop Pairs (133800) | DSPs (740) | Bonded IOB (500) | BUFCTRL (32) |
|---------------------------|---------------------|--------------------------|---------------|-----------------------|------------------------------|------------|------------------|--------------|
| DSP48A1 | 288 | 179 | 122 | 288 | 25 | 1 | 327 | 1 |
| a1reg (reg_mux_input_... | 0 | 18 | 7 | 0 | 0 | 0 | 0 | 0 |
| b1reg (reg_mux_input_... | 0 | 36 | 16 | 0 | 0 | 0 | 0 | 0 |
| carryinreg (reg_mux_in... | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| carryoutreg (reg_mux_i... | 0 | 2 | 1 | 0 | 0 | 0 | 0 | 0 |
| creg (reg_mux_input_... | 0 | 48 | 12 | 0 | 0 | 0 | 0 | 0 |
| dreg (reg_mux_input_... | 0 | 18 | 11 | 0 | 0 | 0 | 0 | 0 |
| mreg (reg_mux_input_... | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| opmodereg (reg_mux_... | 287 | 8 | 87 | 287 | 0 | 0 | 0 | 0 |
| preg (reg_mux_input_... | 0 | 48 | 14 | 0 | 0 | 0 | 0 | 0 |

utilization_2